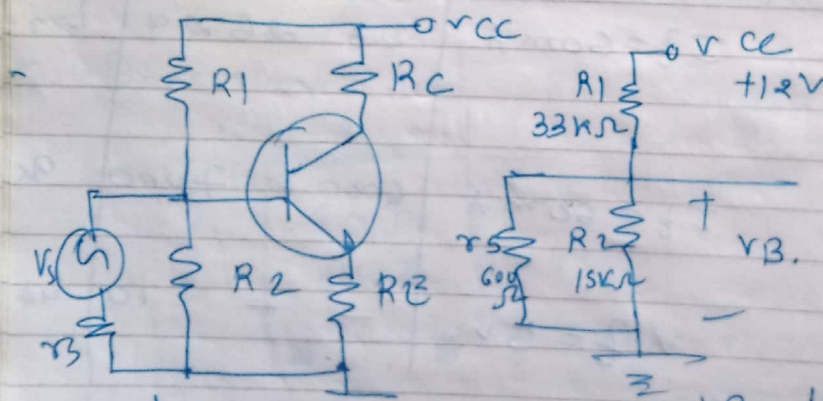


Unit - 4 AC analysis of BJT circuits & small signal amplifiers.

- A transistor circuit used as an ac amplifier normally has the signal source capacitor coupled to the circuit i/p terminal.
- A load resistor at the output is also usually capacitor-coupled to the circuit.
- Capacitor-coupling ensures that the source and load do not affect the dc bias conditions in the circuit.


* Coupling and Bypassing Capacitors.

- To use a transistor circuit to amplify or otherwise process an ac signal, the signal source must be connected to the circuit i/p.
- if the source is directly connected to the i/p, the circuit bias conditions will be altered.



signal source incorrectly direct coupled to the circuit

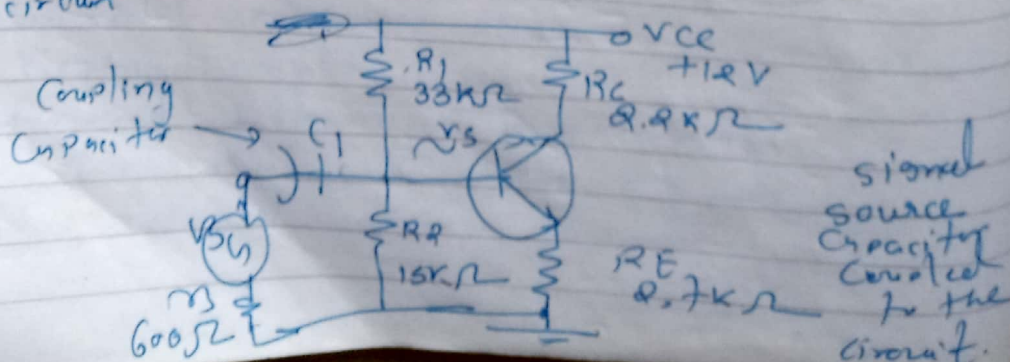
V_B is altered by the dc coupled signal source



for fig. v.

→ Capac for volt bias to be (i is

→ A co at th to c anoth

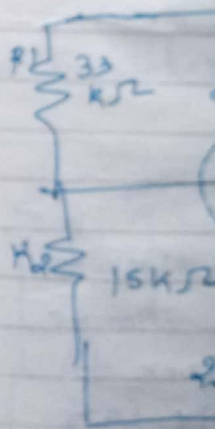

→ The use in fig. co of as an the ac affecting

for fig. 2


$$V_B = \frac{V_{CC} \times (R_1 \parallel R_2)}{R_1 + (R_1 \parallel R_2)}$$

instead of

$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2}$$

→ Capacitor C_1 behaves as a short circuit for the ac signals, so that the signal voltage (V_s) appears at the transistor base. In this case, the signal is said to be ac-coupled to the circuit i/p and C_1 is referred to as a coupling capacitor.

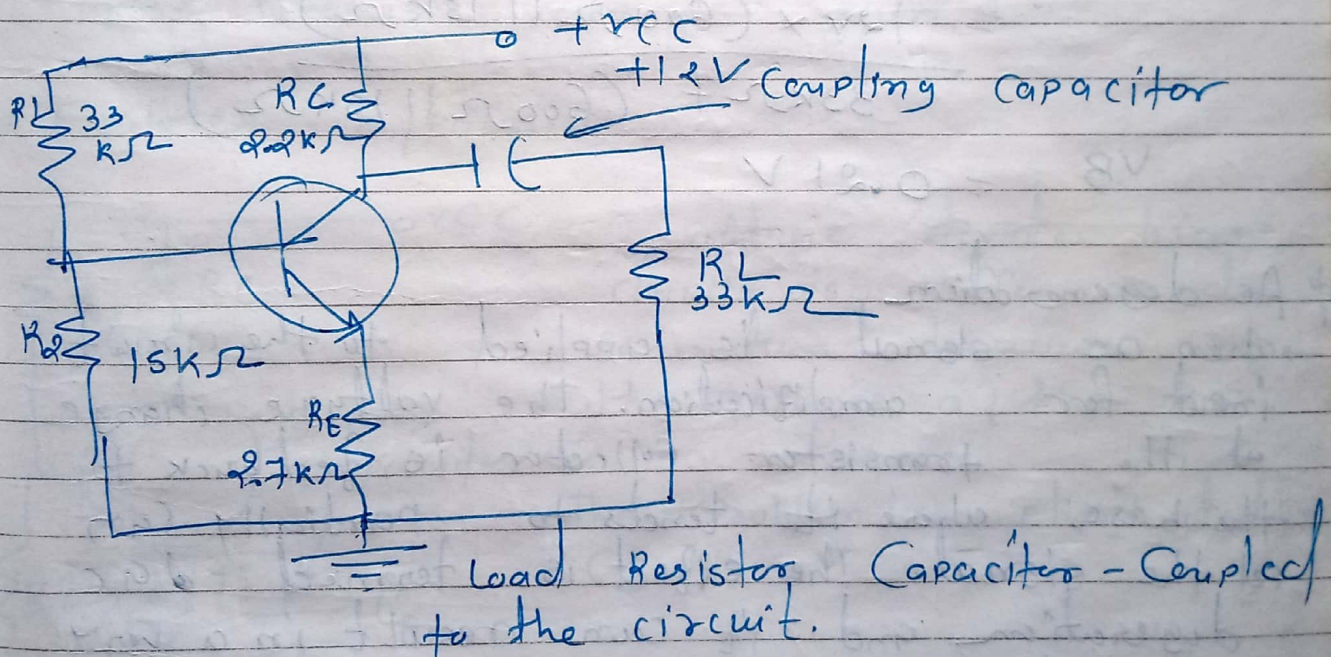→ A coupling capacitor is usually required at the o/p of a transistor circuit to couple to a load resistor or to another amplification stage.



→ The use of an o/p coupling capacitor (C_2) in fig. Like i/p ~~the~~ coupling capacitor, C_2 offers a dc open circuit and behaves as an ac short circuit. Thus, it passes the ac o/p waveform to load w/o affecting the circuit bias conditions.

Ex calculate the base bias voltage for the circuit
 1. c when no signal source is present
 and when the signal source is
 directly connected as in fig 1. a

with no signal source

$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2} = \frac{12V \times 15k\Omega}{33k\Omega + 15k\Omega}$$

$$= 3.75V$$

with the signal source directly connected


$$V_B = \frac{V_{CC} \times (R_2 || R_L)}{R_1 + (R_2 || R_L)}$$

$$= \frac{12V \times (600\Omega || 15k\Omega)}{33k\Omega + (600\Omega || 15k\Omega)}$$


$$V_B = 0.21V$$

* Ac degeneration

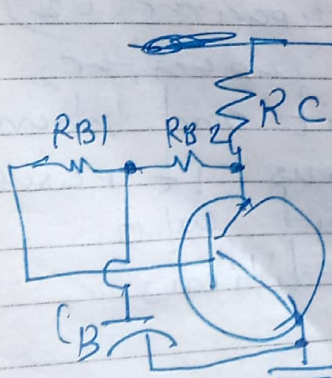→ when ac signal is applied to the circuit
 input for amplification. The voltage change
 at the transistor collector is fed back to
 the base, where it tends to partially can-
 cel the signal. The effect is termed ac
 degeneration and it can result in a very
 low voltage gain.



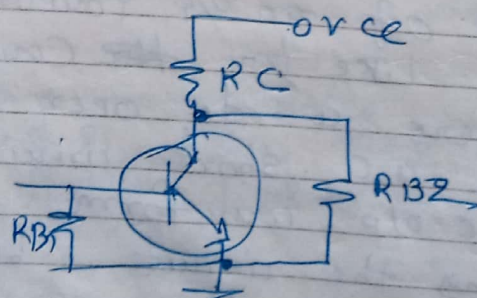Bypass capacitor used with collector to base bias



The bypass capacitor in a ac short circuit


fig shows how ac degeneration is eliminated in CB bias circuit. R_B is replaced with two approximately equal resistors (R_{B1} and R_{B2}), which add up to R_B . Bypass Capacitor (C_B) is connected from the junction of R_{B1} and R_{B2} to the ground terminal.

→ Capacitor C_B offers a short circuit to ac signals, so that there is no feedback from the transistor collector to ^{the} base.

→ C_B is replaced with a short circuit, R_{B1} and R_{B2} appear in parallel with ~~the~~

→ large value resistors, so they do not affect the circuit voltage gain.

* Emitter Bypassing

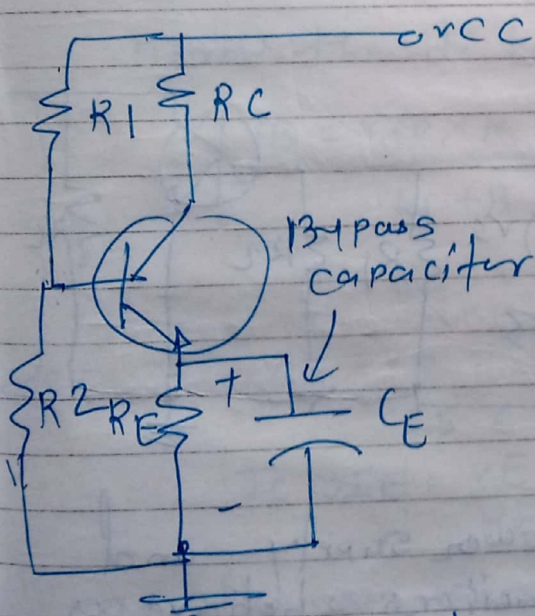

voltage divider bias circuits also suffer ac degeneration because of the presence of the R_E .

The problem is eliminated by C_E

* Capacitor polarity
for the proper operation of the circuit, polarities of the capacitors must be connected correctly. The curve bar which indicates -ve terminal must always be connected at d.c. voltage level lower than (or equal to) the d.c. level of +ve terminal (stomish bc)



* Ac load line

→ capacitors behave as short circuit to ac signals, so in the ac equivalent circuit for a transistor circuit all capacitors must be replaced with short circuits.

→ All the Power Supplies have large value capacitors at o/p terminals and these will offer short circuits to ac signals.

→ so short circuits for power supplies and bypass capacitors give Ac equivalent circuit.

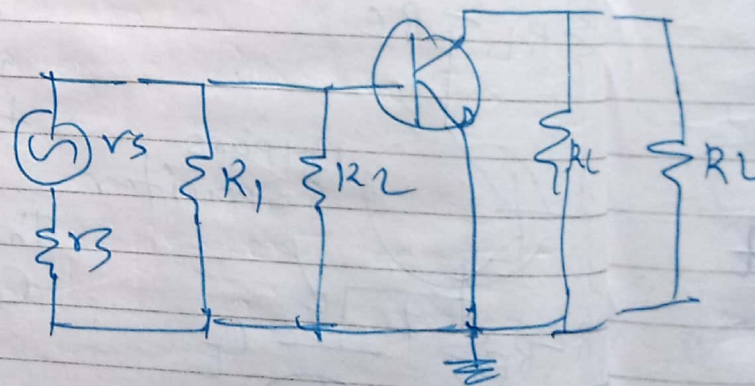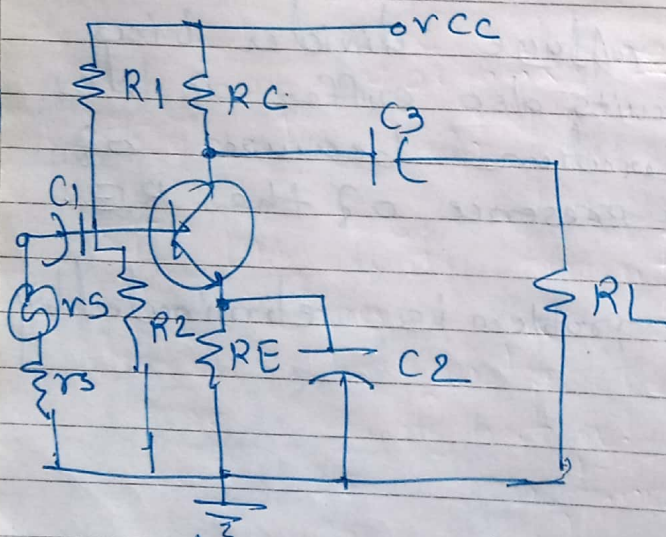→ after that circuit Ac Performance can be investigated by drawing an ac load line and by substituting transistor model for the device.



Circuit with coupling and bypass capacitors

Power supply and capacitors behave as ac short circuits.


→ the dc load for the circuit is $(R_C + R_E)$.

→ Ac load is $R_C || R_L$.

* draw the dc and ac load lines for the transistor circuit in fig. using the transistor common-emitter char. show in fig.

→ Drawing the dc load line:
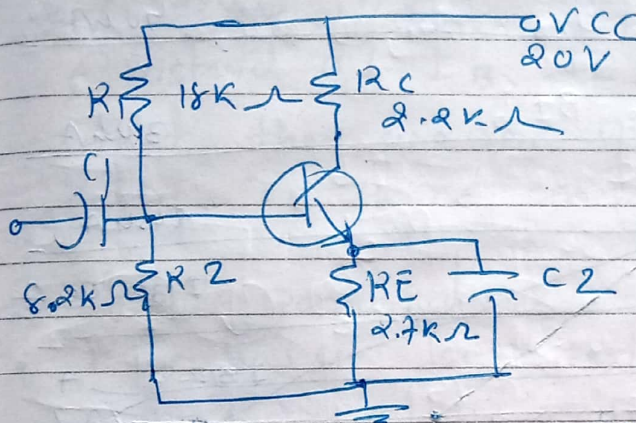
$$R_L(dc) = R_C + R_E = 2.2k + 2.7k = 4.9k$$



$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

when $I_C = 0$

$$V_{CE} = V_{CC} = 20V \quad (\text{point A})$$

$$\text{when } V_{CE} = 0, I_C = \frac{V_{CC}}{R_C + R_E} = \frac{20V}{4.9k} = 4.08mA \quad (\text{point B})$$

Draw the dc load line through A and B

$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2} = \frac{20V \times 8.2k}{18k + 8.2k} = 6.3V$$

$$V_E = V_B - V_{BE} = 6.3V - 0.7V = 5.6V$$

$$I_C \approx I_E = \frac{V_E}{R_E} = \frac{5.6V}{2.7k} = 2.07mA$$

mark the α point on the dc load line at $I_C = 2.07mA$


→ Drawing the ac load line when there is no external R_L

$$R_L(ac) = R_C = 2.2k$$

$$\Delta I_C = 2.07mA$$

$$\Delta V_{CE} = \Delta I_C \times R_C = 2.07mA \times 2.2k$$

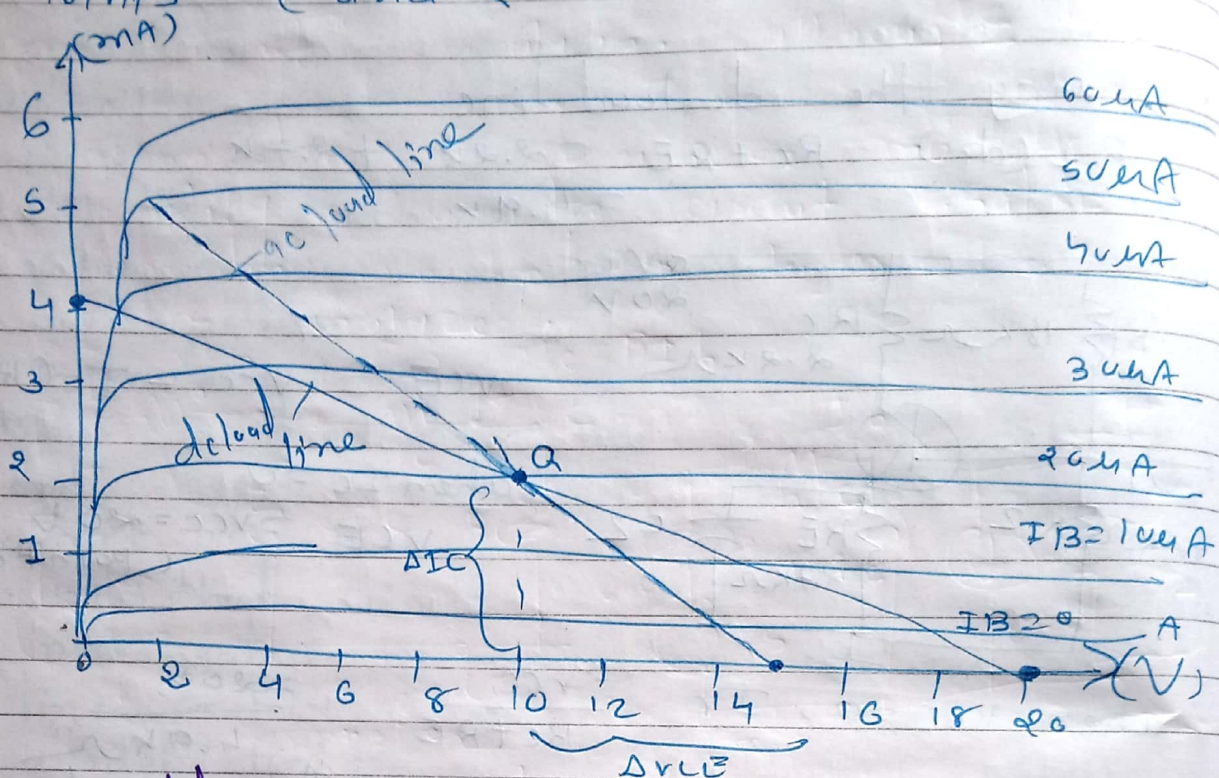plot point c at $\Delta I_C = 2.07 \text{ mA}$ and $\Delta V_{CE} = 4.55 \text{ V}$ from the Q point.
 → Draw the ac load line through points C and Q



O/p voltage swing

$$V_{oc(max)} \approx 4.5 \text{ V}$$

* Transistor Models and Parameters

T Equivalent circuit



→ fig shows the ac equivalent circuit for a transistor connected in common-base configuration.

r_e - BE resistance

r_c - CB resistance

r_b - base region resistance

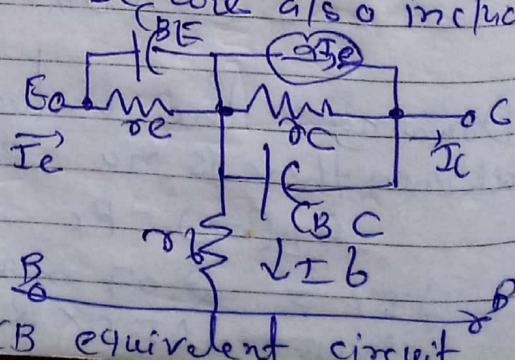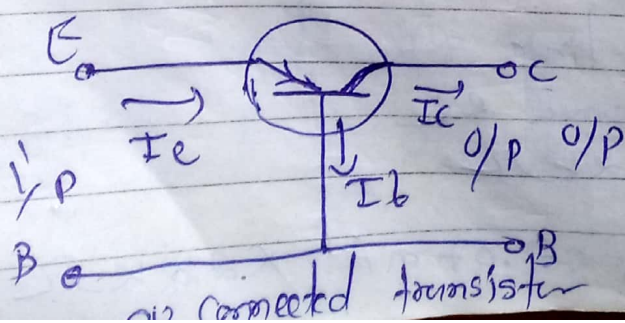Junction capacitance C_{BE} & C_{BC} are also included



→ current generator is included in parallel with r_c and C_{BC} .



$$\alpha = I_C / I_E$$

→ complete circuit is known as the T-equivalent circuit, or the r -parameter equivalent circuit.

→ currents in fig are designated I_b, I_c and I_e (instead of I_B, I_C and I_E) to indicate that they are ac quantities rather than dc. r_c, r_b, r_e and α are also ac quantities.

→ r -parameters

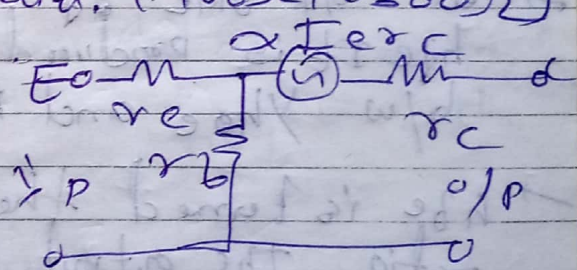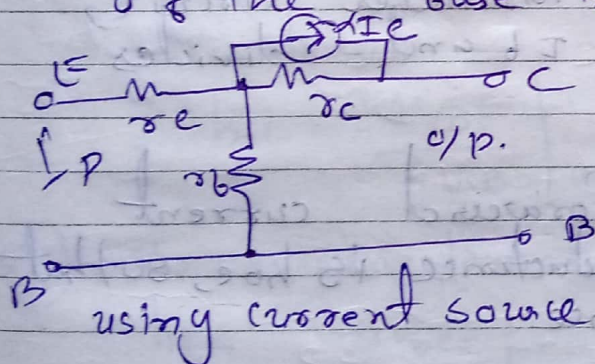
- r_e has a low resistance value because (typically 25Ω)
- r_c has a high resistance value (typically $100 k\Omega$ to $1 M\Omega$)
- r_b depends upon the doping density of the base material. (about 200Ω)



Determination of r_e


→ it can be determined from a plot of I_E versus V_{BE}
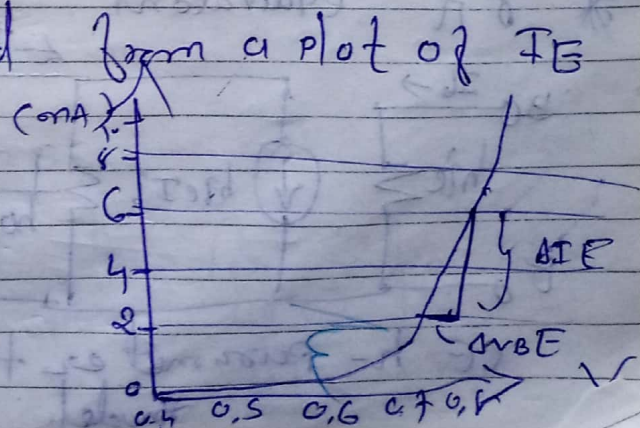
$$r_e = \frac{\Delta V_{BE}}{\Delta I_E}$$



h-parameters
 → The hybrid parameters (or h parameters) are much more convenient for circuit analysis. These are used only for ac circuit analysis, although dc

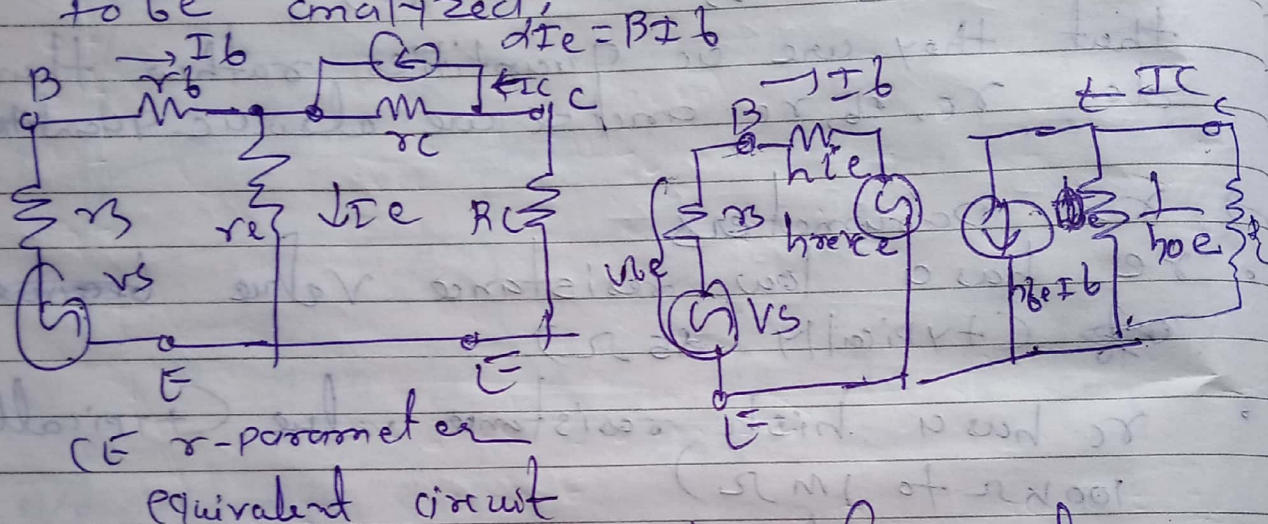
Transistor h-parameter models simplify transistor circuit analysis by separating i/p and o/p stages of a circuit to be analyzed.



→ h_{re} is reverse voltage transfer ratio
 → at o/p side of h-parameter circuit, $h_{re} I_B$ is produced by I_B and divides b/w Y_{hoe} and R_C .

→ h_{fe} is termed the forward current ratio. The output conductance is h_{oe} , so that Y_{hoe} is a resistance.

* π equivalent circuit

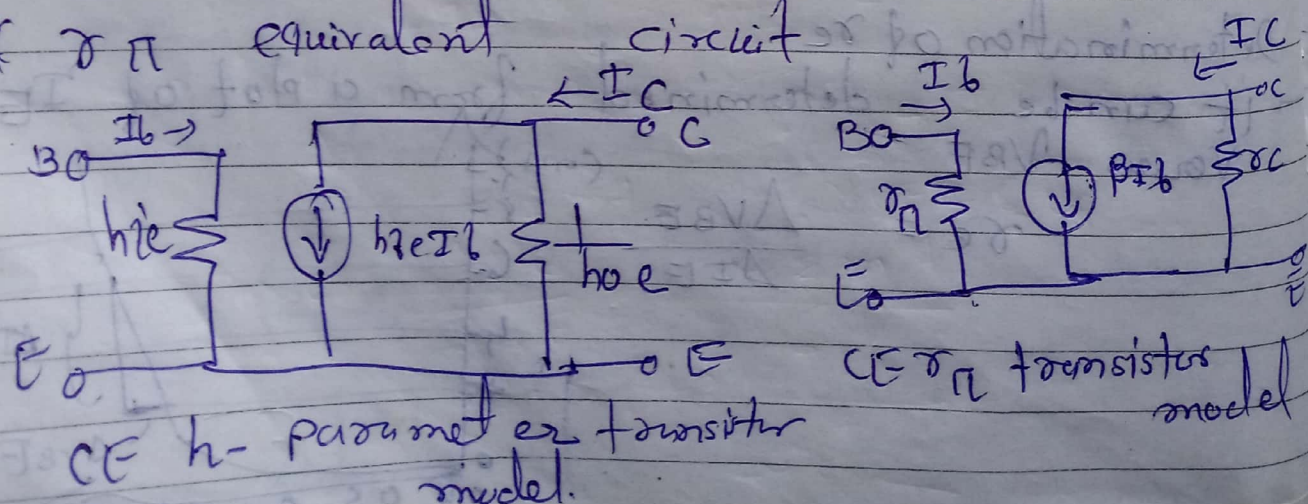

in fig.1 feedback generator ($h_{ro} v_{ce}$) is omitted. The effect of $h_{ro} v_{ce}$ is very small so it can be neglected.

→ This approximate h-parameter circuit is reproduced in fig.2 with the components labelled as π -parameters $r_{\pi} = h_{ie}$, $\beta I_b = h_{fe} I_b$, $r_c = h_{oe}$. This circuit is known as a hybrid π model, is sometimes used instead of the h-parameter circuit.

→ Definition of h-Parameters

one h_{ie} (i-input, e-common emitter)


1) Ac i/p resistance h_{ie} defined as the ac i/p voltage divided by the ac i/p current.

$$h_{ie} = \frac{V_{be}}{I_b}$$

$$h_{ie} = \frac{V_{be}}{I_b} \bigg|_{V_{ce}}$$

at dc level

$$h_{ie} = \frac{\Delta V_{BE}}{\Delta I_B} \bigg|_{V_{CE}}$$

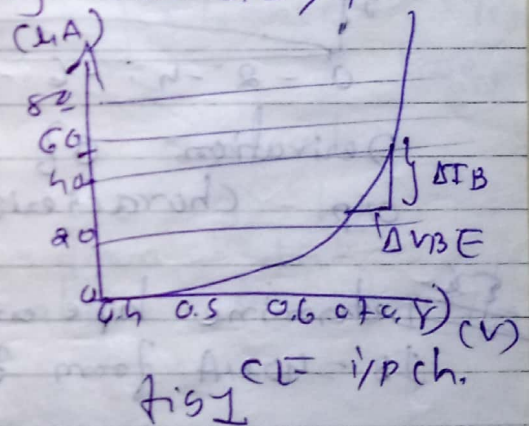

2) The reverse transfer ratio


$$h_{oe} = \frac{\Delta V_{be}}{\Delta V_{ce}} \bigg|_{I_b}$$

for dc

$$h_{oe} = \frac{\Delta V_{BE}}{\Delta V_{CE}} \bigg|_{I_B}$$

3) The forward current transfer ratio h_{fe}

$$h_{fe} = \frac{I_C}{I_B} \bigg|_{V_{CE}} \quad \text{or} \quad \frac{\Delta I_C}{\Delta I_B} \bigg|_{V_{CE}}$$

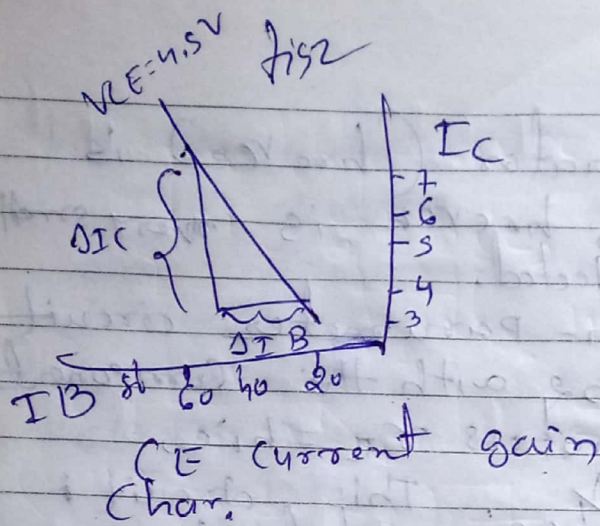


4) output conductance h_{oe}

$$h_{oe} = \left. \frac{I_C}{V_{CE}} \right|_{I_B}$$

or

$$h_{oe} = \left. \frac{\Delta I_C}{\Delta V_{CE}} \right|_{I_B}$$

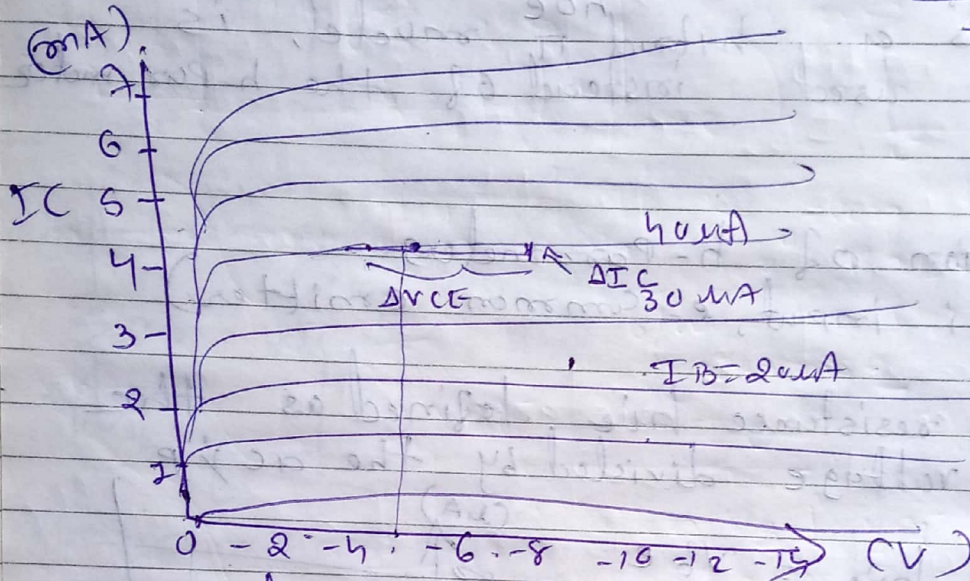

Derivation of h_{oe} from the CE o/p characteristics.

Ex Determine h_{fe} and h_{oe} for $V_{CE} = 4.5V$ and $I_B = 40\mu A$ from fig 2 and 3

$$V_{CE} = 4.5V, \quad I_B = 40\mu A$$

$$\Delta I_C = 4mA, \quad \Delta I_B = 30\mu A$$

$$h_{fe} = \frac{\Delta I_C}{\Delta I_B} = \frac{4mA}{30\mu A} = 133$$

from o/p ch. fig. 3 $V_{CE} = 4.5V, \quad I_B = 40\mu A$

$$\Delta I_C = 0.2mA, \quad \Delta V_{CE} = 6V$$

$$h_{oe} = \frac{\Delta I_C}{\Delta V_{CE}} = \frac{0.2mA}{6V}$$

$$= 33.3 \mu S$$

$$\frac{1}{h_{oe}} = \frac{1}{33.3 \mu S} = 30k\Omega$$

* Parameter relationships

In datasheets only CE h-parameters are stated. However CB and CC h-parameters can be determined from the CE h-parameters. α parameters can also be calculated from the CE h-parameters.

CE to CB
h-parameters

$$h_{ib} \approx \frac{h_{ie}}{1+h_{ie}}$$

$$h_{rb} \approx \frac{h_{ie}h_{oe}}{1+h_{ie}} - h_{re}$$

$$h_{fb} \approx \frac{h_{fe}}{1+h_{fe}}$$

$$h_{ob} \approx \frac{h_{oe}}{1+h_{fe}}$$

CE to CC
h parameters

$$h_{ic} = h_{ie}$$

$$h_{rc} = 1 - h_{re}$$

$$h_{fc} =$$

$$h_{fc} = 1 + h_{fe}$$

$$h_{oc} = h_{oe}$$

CE h-parameters
to α -parameters

$$\alpha \approx \frac{h_{fe}}{1+h_{fe}}$$

$$r_c = \frac{1+h_{fe}}{h_{oe}}$$

$$r_e = \frac{h_{ie}}{1+h_{fe}} \approx r_d$$

$$r_b = h_{ie} - h_{re} \left(\frac{1+h_{fe}}{h_{oe}} \right)$$

$$r_n = h_{ie}$$

$$\beta = h_{fe}$$


Ex calculate h_{fc} , h_{ob} and α from the parameters determined in above example.

$$h_{fc} = 1 + h_{fe} = 1 + 133 = 134$$





$$h_{ob} \approx \frac{h_{oe}}{1+h_{fe}} \approx \frac{33.3 \mu S}{1+133} = 249 nS$$

$$\alpha \approx \frac{h_{fe}}{1+h_{fe}} \approx \frac{133}{1+133} = 0.993$$

Common - Emitter circuit analysis

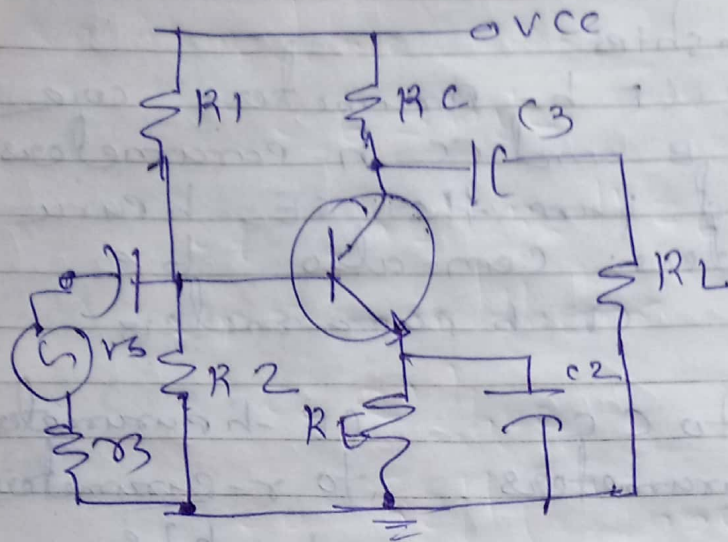

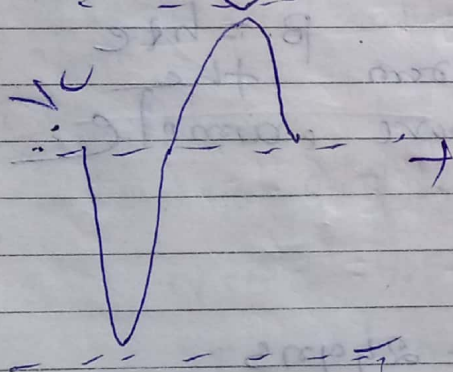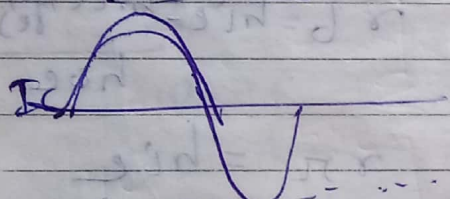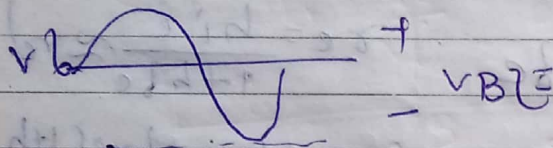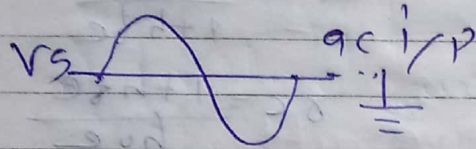current and voltage waveforms for the CE circuit are illustrated in fig.




it is seen that there is a 180° phase shift b/w the i/p and o/p waveforms.


→ when $V_S \uparrow$ $V_{BE} \uparrow$ $I_C \uparrow$ there by increasing the voltage drop across R_C , then $V_C \downarrow$. V_C capacitor coupled to o/p

→ So as V_S increases in +ve direction, V_O goes in -ve direction, same vice versa.

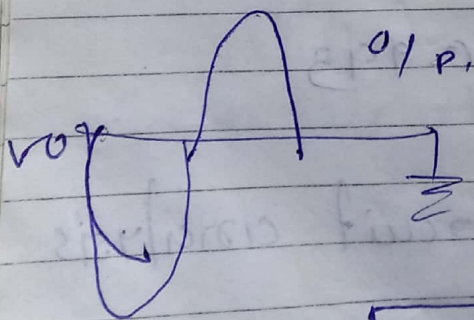→ The circuit has i/p impedance Z_i and o/p impedance (Z_o)




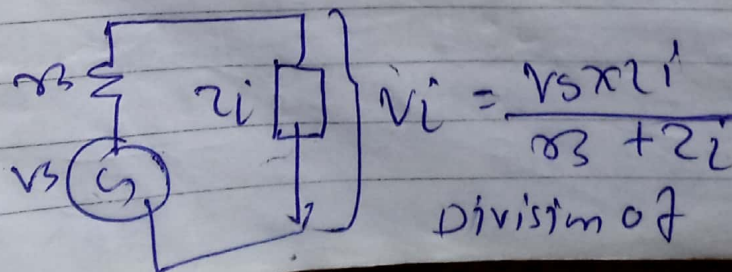→ voltage gain depends on the transistor parameters and on resistors R_C and R_L




$$V_i = \frac{V_S \times Z_i}{R_S + Z_i}$$

Division of signal voltage

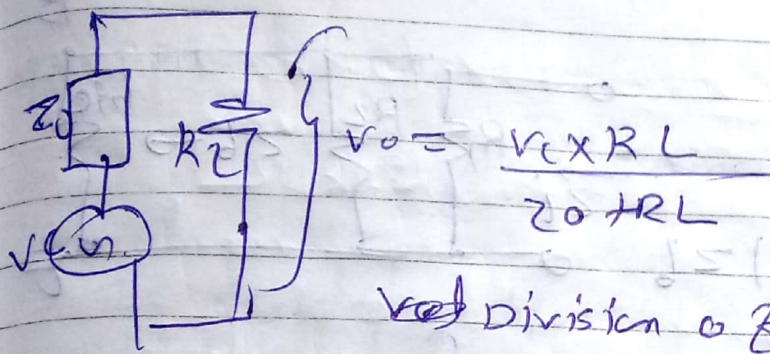


Voltage Division of a/c voltage

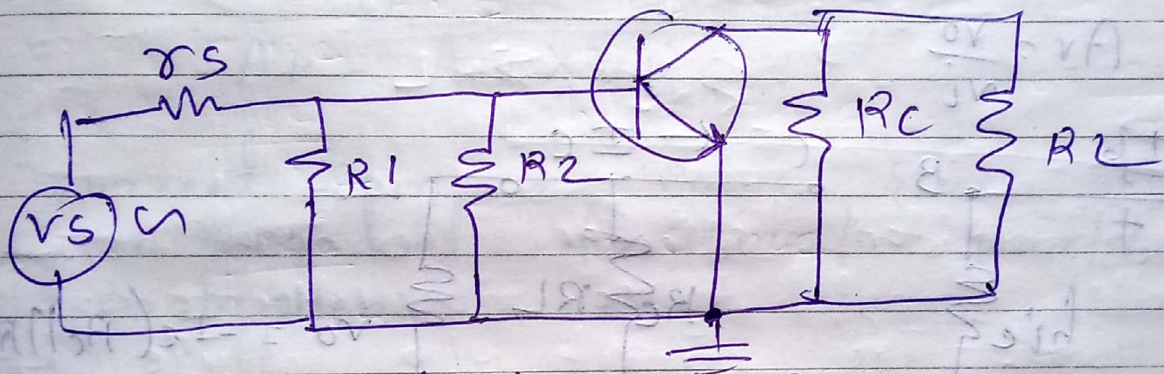→ The first step in ac analysis of a Transistor circuit is to draw the ac equivalent circuit, by placing short circuits in place of power supply and Capacitors.



ac equivalent cir. for CE trans. circ.

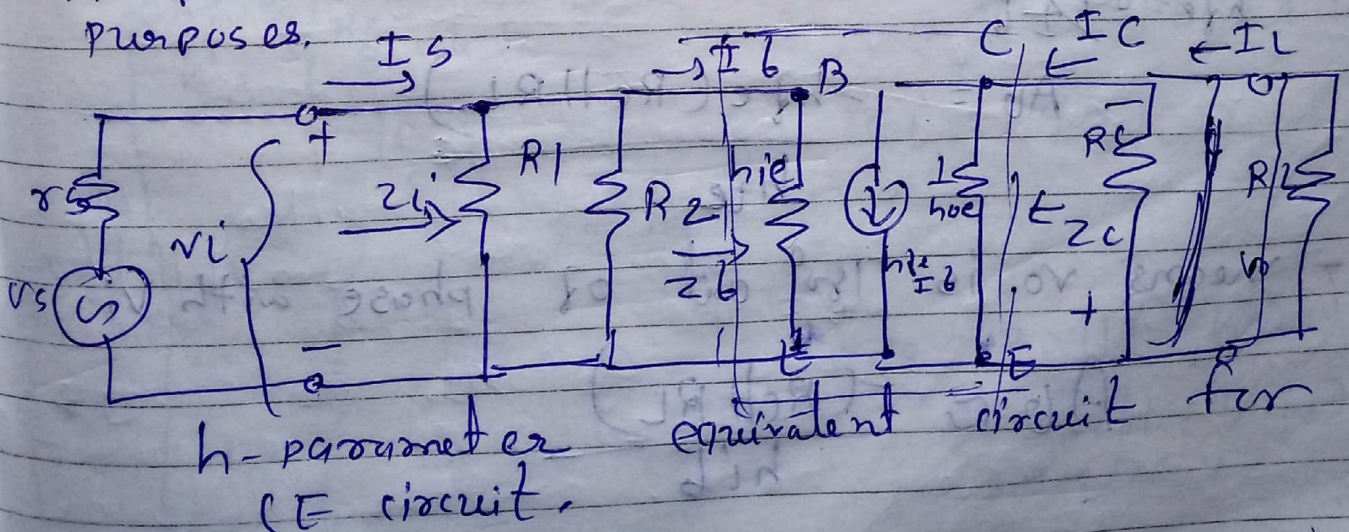
→ Now replace transistor in ac. equivalent circuit with its h-parameter model. This gives CE-h parameter equivalent circuit. Note that $h_{re} V_C$ is omitted because its effect is unimportant for most practical purposes.



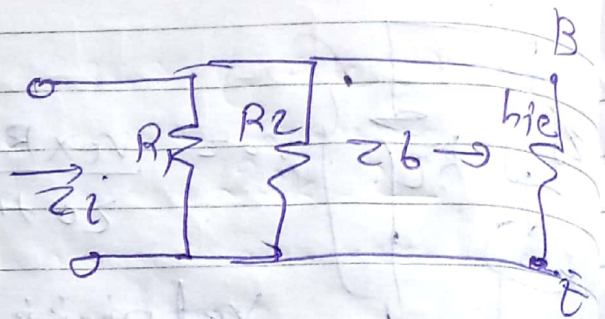1) i/p impedance

$$Z_b \approx h_{ie}$$


$$Z_i = R_1 \parallel R_2 \parallel Z_b$$



2) o/p impedance


$$Z_c \approx 1/h_{oe}$$

$$Z_o = R_c \parallel (1/h_{oe})$$

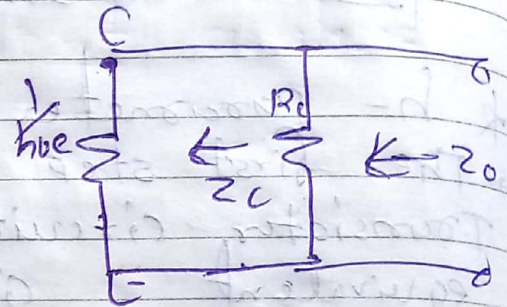

3) voltage gain

$$A_v = \frac{v_o}{v_i}$$

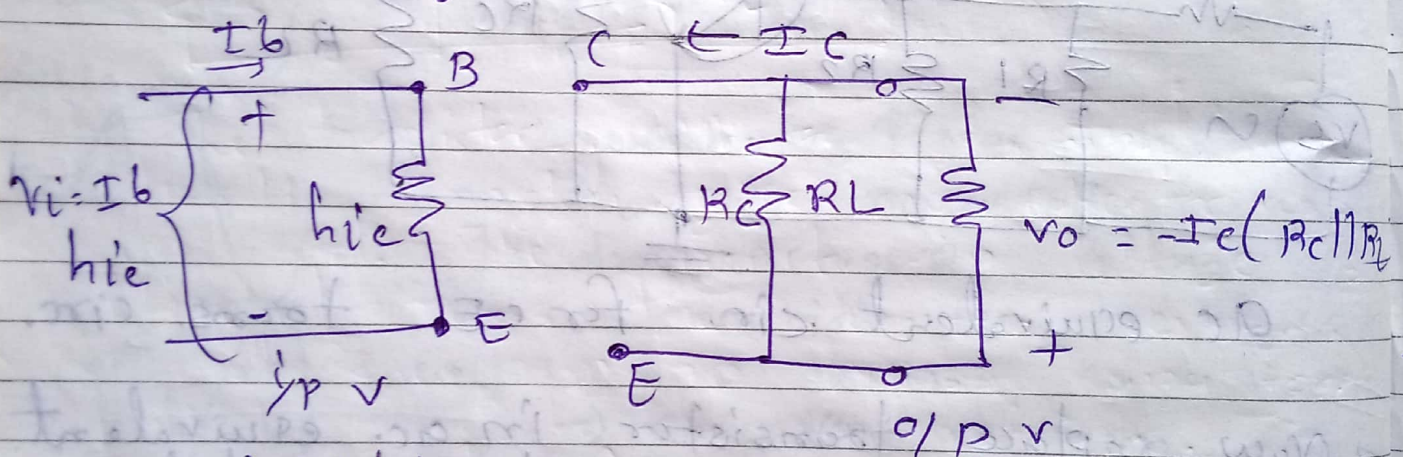

$$v_i = I_b h_{ie}, v_o = -I_c (R_c \parallel R_L)$$

$$A_v = \frac{-I_c (R_c \parallel R_L)}{I_b h_{ie}}$$

$$h_{fe} = I_c / I_b$$

$$A_v = \frac{-h_{fe} (R_c \parallel R_L)}{h_{ie}}$$

- means v_o is 180° out of phase with v_i

$$A_v \approx \frac{-(R_c \parallel R_L)}{h_{ib}}$$

* current gain

$$h_{fe} = \frac{I_c}{I_b} \quad (\text{Transistor ac current gain})$$

I_s divided b/w h_{ie} and bias resistors
 I_c divided b/w R_c and R_L

overall circuit current gain


$$A_i = \frac{h_{fe} R_c R_B}{(R_c + R_L)(R_c + h_{ie})}$$

* Power Gain

$$A_p = A_v \times A_i$$

current gain & power gain largely unimportant for most practical applications.

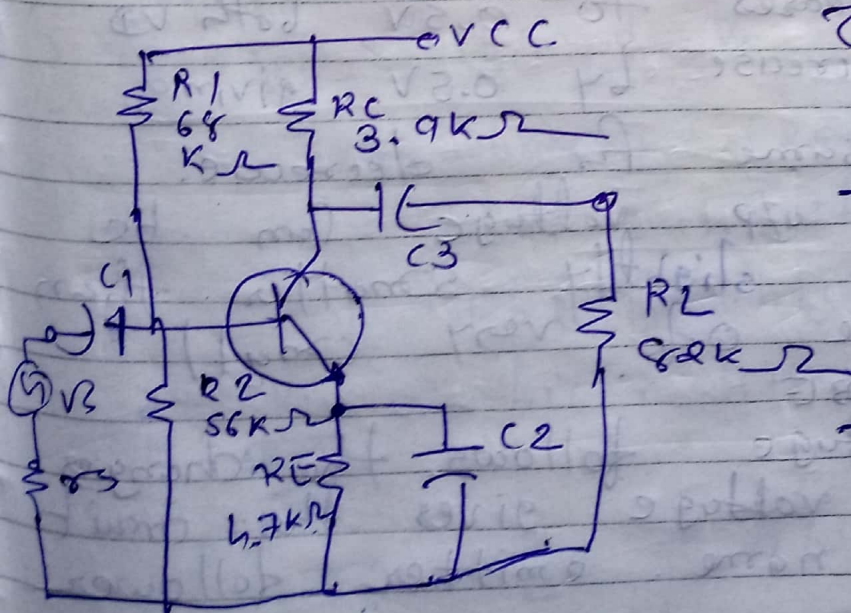ex The transistor in the CE circuit in fig has the following parameters; $h_{ie} = 2.1 \text{ k}\Omega$, $h_{fe} = 75$, $h_{oe} = 1 \mu\text{S}$. Calculate the circuit i/p impedance, o/p impedance, and voltage gain.



$$\begin{aligned} \tau_i &= R_1 \parallel R_2 \parallel h_{ie} \\ &= 68 \text{ k}\Omega \parallel 56 \text{ k}\Omega \parallel 2.1 \text{ k}\Omega \end{aligned}$$


$$\tau_i = 1.97 \text{ k}\Omega$$

$$\begin{aligned} \tau_o &= R_c \parallel (1/h_{oe}) \\ &= 3.9 \text{ k}\Omega \parallel (1/1 \mu\text{S}) \\ &= 3.9 \text{ k}\Omega \end{aligned}$$

$$A_v = \frac{-h_{fe}(R_C \parallel R_L)}{h_{ie}} = \frac{-75 \times (3.9k\Omega \parallel 18.2k\Omega)}{2.1k\Omega}$$

$$= -133$$

Common - collector circuit analysis

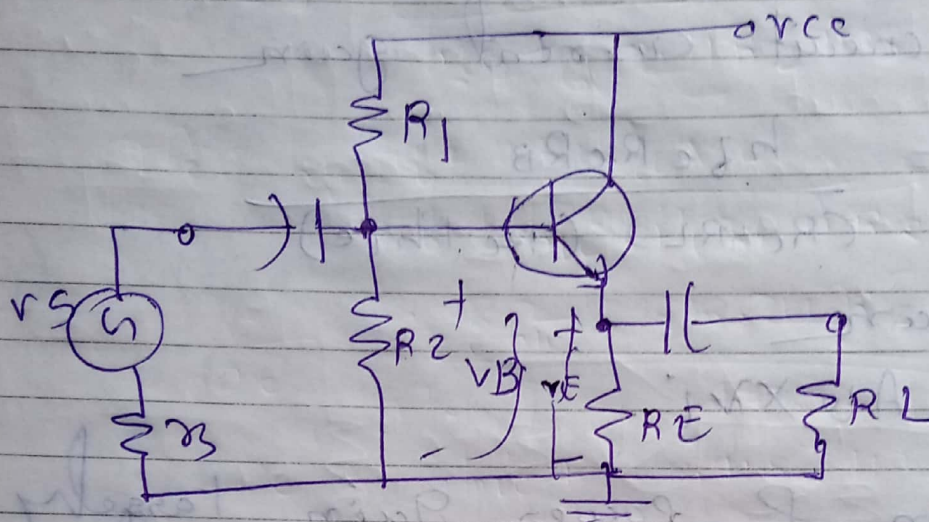


→ The transistor collector terminal is directly connected to v_{cc} . no collector resistor is used. The circuit o/p voltage is developed across the emitter resistor (R_E) and there is no bypass capacitor.

$$\begin{matrix} v_s \uparrow & V_B \uparrow & V_E \uparrow & (V_E = V_B - V_{BE}) \\ v_o \uparrow & & & V_{BE} \text{ is constant} \end{matrix}$$


→ when v_s increases to 0.5V, both V_B and V_E increase by 0.5V, giving $v_o = 0.5V$ same for decrease.

→ Actually the o/p voltage can be shown to be slightly smaller than the i/p because of very small change in V_{BE} .

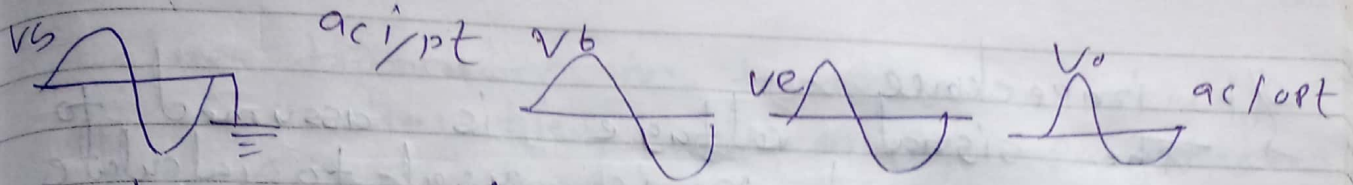
→ cc o/p voltage follows the change in signal voltage gives the circuit its other name: emitter follower



* h-parameter equivalent circuit.

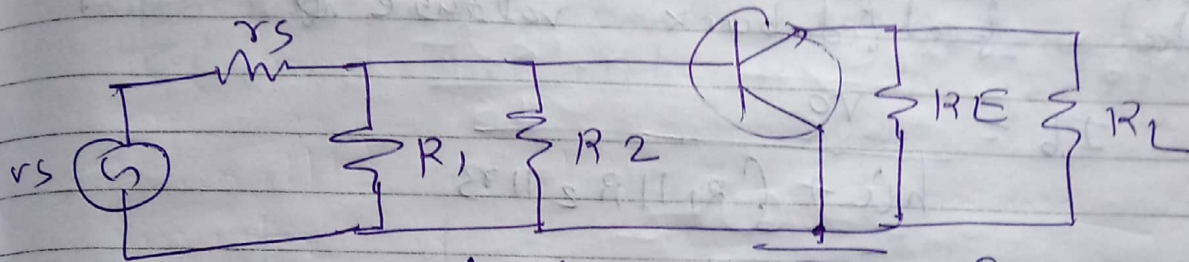

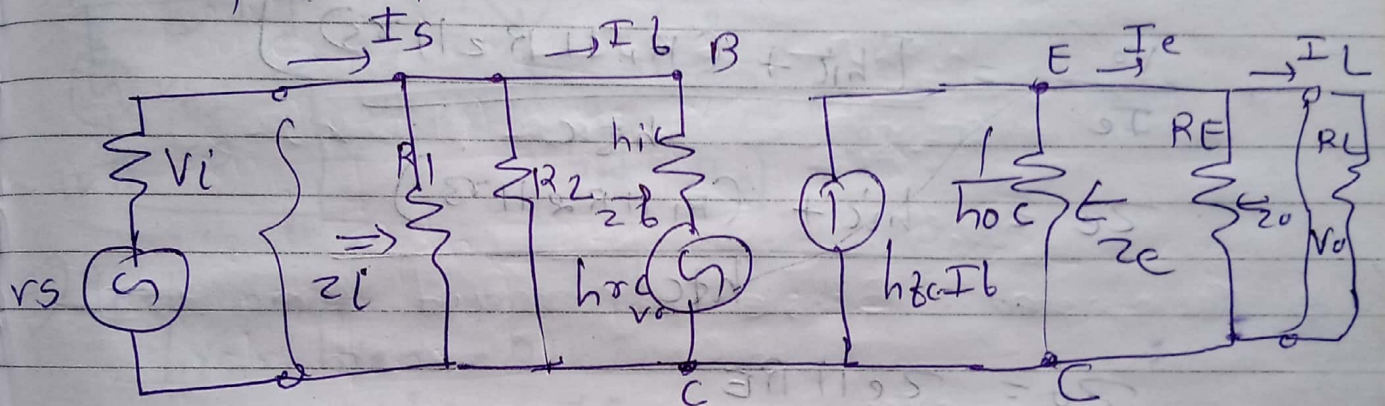A c equivalent circuit for c.c transistor circuit



all of v_o is fed back to the i.p. so, unlike the case of CE circuit, the feedback generator cannot be omitted in the equivalent circuit of CC amplifier

1) p impedance

$$V_i = I_b h_{ie} + h_{oc} V_o \quad (h_{oc} = 1)$$

$$= I_{bhic} + I_e (R_E || R_L)$$

$$= I_{b_{hie}} + h_{fe} I_b (R_E \parallel R_L)$$

$$V_1' = I_b [h_{ic} + h_{fc}(R_E || R_L)]$$

$$\frac{v_i'}{\gamma \beta} = h_{ic} \neq h_{ic} (R_E || R_L)$$

$$Z_b = h_{ic} + h_{fc} (R_E || R_L)$$

$$Z_i = R_1 || R_2 || Z_L$$

o/p impedance
 → The signal voltage is assumed to be zero, and v_o is used to calculate I_e . with $v_s = 0$, I_b is produced by the ~~test~~ feedback voltage @

$$I_b = \frac{v_o}{h_{ic} + (R_1 \parallel R_2 \parallel r_s)}$$

$$I_e = h_{fc} I_b = \frac{h_{fc} v_o}{h_{ic} + (R_1 \parallel R_2 \parallel r_s)}$$

$$\frac{v_o}{I_e} = \frac{h_{fc}}{h_{ic} + (R_1 \parallel R_2 \parallel r_s)}$$

$$Z_e = \frac{h_{ic} + (R_1 \parallel R_2 \parallel r_s)}{h_{fc}}$$

$$Z_o = Z_e \parallel R_E$$

Voltage gain

o/p voltage from c.c. circuit is almost exactly equal to the i/p voltage.

$$V_i = I_b [h_{ic} + h_{fc} (R_E \parallel R_L)]$$

$$v_o = I_e (R_E \parallel R_L)$$


$$A_v = \frac{v_o}{V_i} = \frac{I_e (R_E \parallel R_L)}{I_b [h_{ic} + h_{fc} (R_E \parallel R_L)]}$$

$$A_v = \frac{(R_E \parallel R_L)}{h_{ic} + (R_E \parallel R_L)}$$

$R_E \parallel R_L$ is so much larger than h_{ic} so

$$A_v \approx 1$$

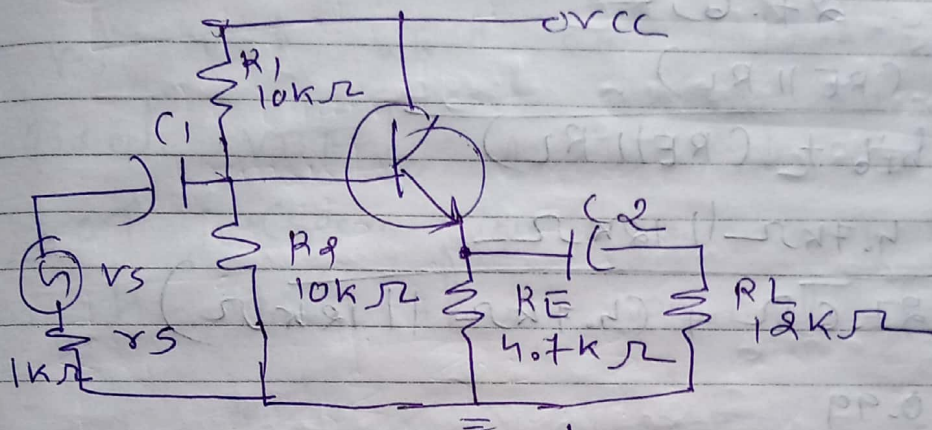Ex The transistor in the cc circuit in fig has the following parameters $h_{ie} = 2.1 k\Omega$ and $h_{fe} = 75$. (a) calculate the circuit i_{pp} and o/p impedance with R_L not connected, (b) calculate Z_i and A_v with R_L connected.



9) R_L is not connected

$$h_{ic} = h_{ie} = 2.1 k\Omega$$

$$h_{fc} = 1 + h_{fe} = 76$$

$$Z_b = h_{ic} + h_{fc}(R_E || R_L) = 2.1 k\Omega + 76(4.7 k\Omega) = 359.3 k\Omega$$

$$Z_i = R_1 || R_2 || Z_b = 10 k\Omega || 10 k\Omega || 359.3 k\Omega = 4.93 k\Omega$$

$$Z_e = \frac{h_{ic} + (R_1 || R_2 || r_s)}{h_{fc}} = \frac{2.1 k\Omega + (10 k\Omega || 10 k\Omega || 1 k\Omega)}{76}$$

$$Z_e = 38.6 \Omega$$

$$Z_o = Z_e || R_E = 38.6 \Omega || 4.7 k\Omega = 38.3 \Omega$$

b) R_L connected

$$Z_b = h_{ic} + h_{fc}(R_E || R_L) = 2.1 k\Omega + 76(4.7 k\Omega || 12 k\Omega)$$

$$Z_b = 258.8 \text{ k}\Omega$$

$$Z_i = R_1 \parallel R_2 \parallel Z_b$$

$$= 10 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 258.8 \text{ k}\Omega$$

$$= 4.91 \text{ k}\Omega$$

$$h_{ib} = \frac{h_{ie}}{1 + h_{fe}} = \frac{2 \text{ k}\Omega}{1 + 75}$$


$$= 27.6 \Omega$$

$$A_v = \frac{(R_E \parallel R_L)}{h_{ib} + (R_E \parallel R_L)}$$


$$= \frac{4.7 \text{ k}\Omega \parallel 12 \text{ k}\Omega}{27.6 \Omega + (4.7 \text{ k}\Omega \parallel 12 \text{ k}\Omega)}$$

$$= 0.99$$


* Common Base circuit analysis

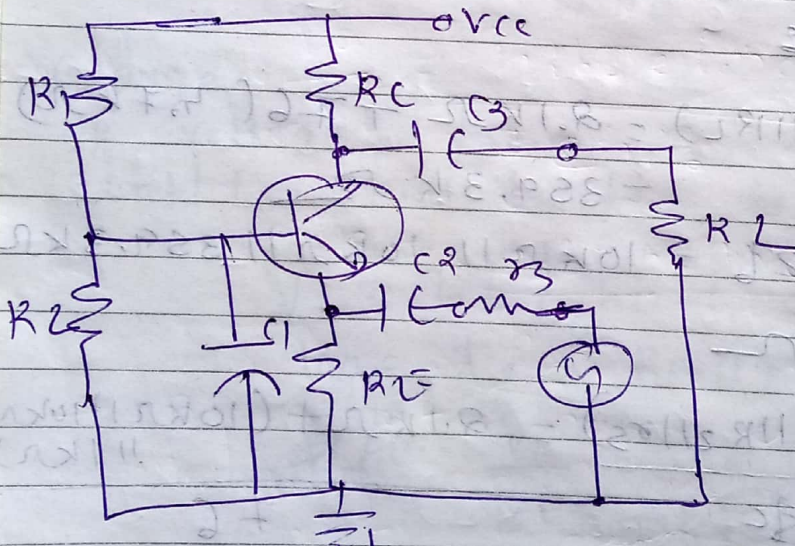

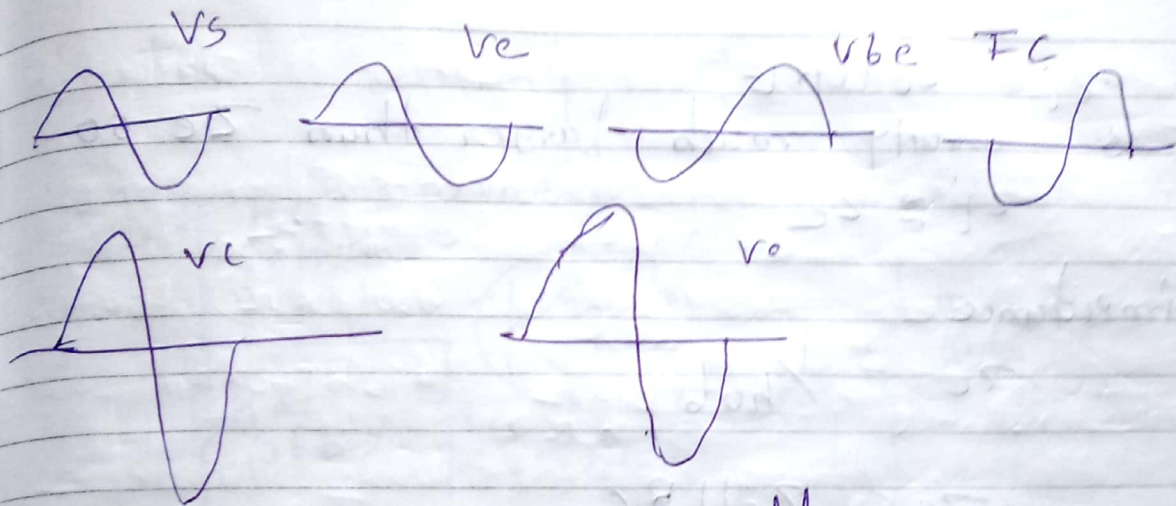
- i/p signal is applied to the transistor emitter terminal (via C_1) instead of base
- there is no bypass capacitor across the R_E , but the base terminal is ac grounded via capacitor C_1 .
- o/p voltage developed across the R_C .



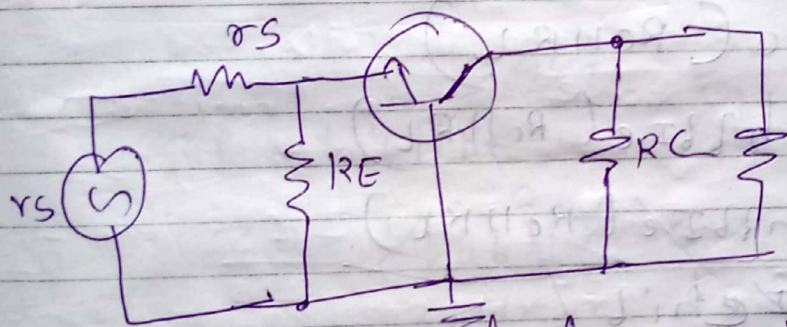$V_s \uparrow \rightarrow V_E \uparrow$, base voltage ~~is~~ remain fixed. $V_{BE} \downarrow \rightarrow I_C \downarrow \rightarrow V_{RC} \downarrow \rightarrow V_C \uparrow$
 $V_O \uparrow$ (seen in the waveform)
 $\rightarrow$ h-parameter equivalent circuit.



ac equivalent circuit for CB

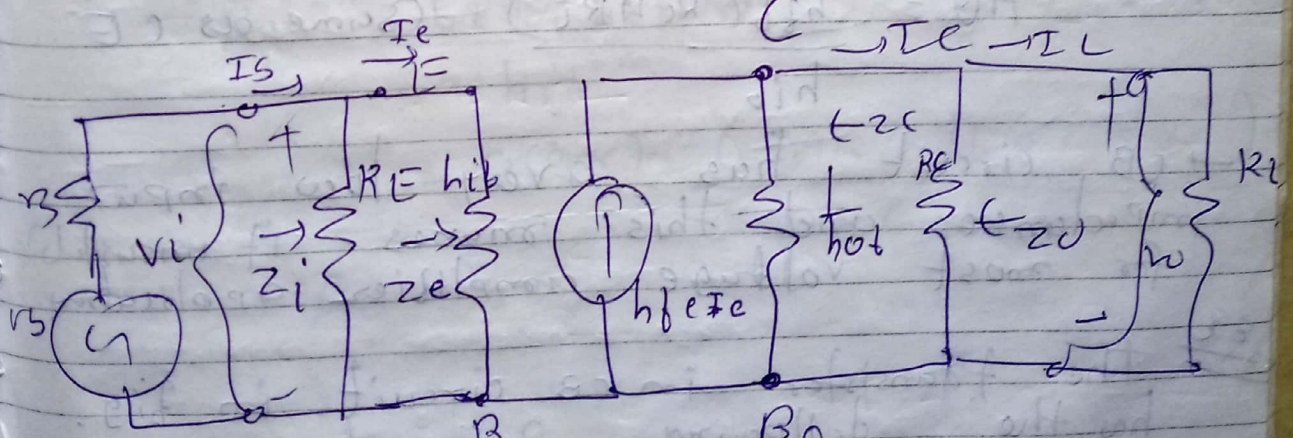

h-parameter AC equivalent circuit for CB

1) Input impedance

$Z_e = h_{ib}$
 h_{ib} is around 21Ω for low current transistor.

$z_i = z_e \parallel R_E$
 R_E is usually much larger than z_e so
 $z_i \approx z_e$

2) i/p impedance

$$z_c = 1/h_{ob}$$

$$z_o \approx z_c \parallel R_C$$

z_c is normally much larger than R_C , $z_o \approx R_C$

3) voltage gain

$$v_i = I_e h_{ie}$$

$$v_o = I_c (R_C \parallel R_L)$$

$$= h_{fe} I_e (R_C \parallel R_L)$$


$$\frac{v_o}{v_i} = \frac{h_{fe} I_e (R_C \parallel R_L)}{I_e h_{ie}}$$

$$A_V = \frac{h_{fe} (R_C \parallel R_L)}{h_{ie}} \quad (\text{Same as CE})$$

→ CB circuit has a very low input impedance, and this makes it unsuitable for most voltage amplifier applications

Ex

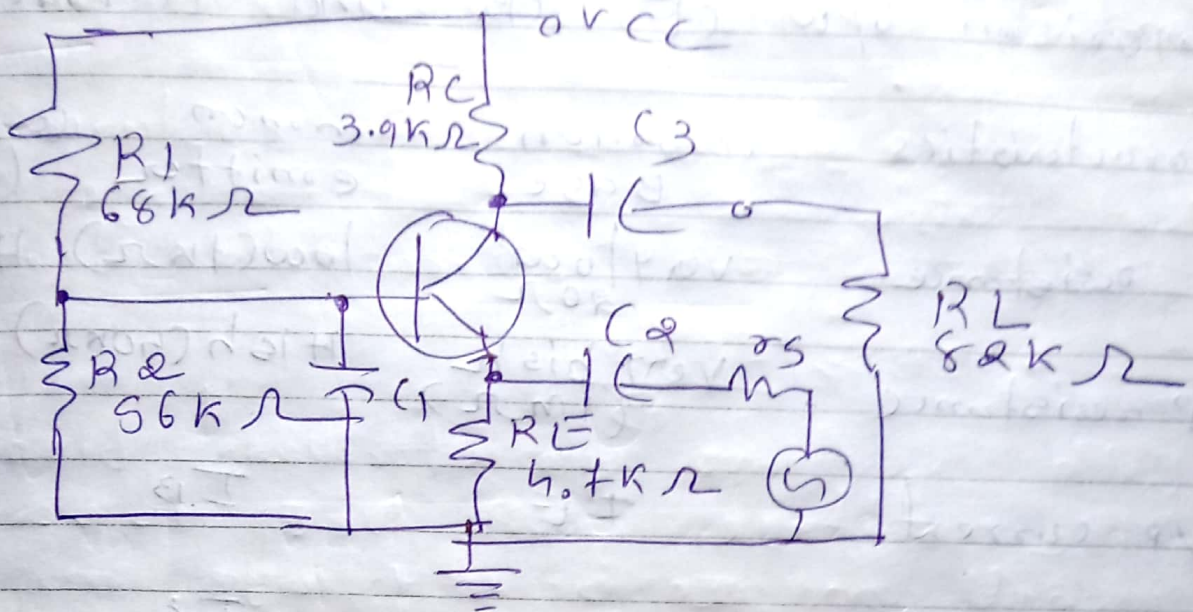The transistor in CB circuit in fig. has the following parameters:
 $h_{ie} = 2.1 \text{ k}\Omega$ and $h_{fe} = 75$. Calculate the circuit i/p and o/p impedances and voltage gain.



$$h_{ib} = \frac{h_{ie}}{1 + h_{fe}} = \frac{2.1k\Omega}{1 + 75} = 27.6\Omega$$

$$h_{fb} = \frac{h_{fe}}{1 + h_{fe}} = \frac{75}{1 + 75} = 0.987$$

$$Z_i = h_{ib} \parallel R_E = 27.4\Omega$$

$$Z_o = R_C \parallel R_L = 3.9k\Omega$$

$$A_v = \frac{h_{fb} (R_C \parallel R_L)}{h_{ib}} = \frac{0.987 (3.9k\Omega \parallel 82k\Omega)}{27.6\Omega}$$

$$A_v = 133$$

* Comparison b/w CE, CB and CC circuits

characteristics	Common Base	Common emitter	Common collector
i/p resistance	very low (20Ω)	low ($1k\Omega$)	High ($50k\Omega$)
o/p resistance	very high ($1M\Omega$)	High ($40k\Omega$)	Low
i/p current	I_E	I_B	I_E
o/p current	I_C	I_C	I_E
i/p voltage applied b/w	Emitter and Base	Base and emitter	Base collector
o/p voltage taken b/w	collector and Base	collector and emitter	emitter collector
current amplification factor	$\alpha = \frac{I_C}{I_E}$	$\beta = \frac{I_C}{I_B}$	$\gamma = \frac{I_E}{I_D}$
current gain	less than unity	High (a few hundreds)	High (a few)
voltage gain	Medium	Medium	Medium
Applications	As a i/p stage of multi stage amplifier	for audio signal amplification	


- * Transistor as a Switch
- Transistor can be used for two types of applications like amplification & switching
- for amplification, transistor is biased in its active region
 - for switching, it is biased to operate

in saturation (fully on) or cutoff (fully off) regions

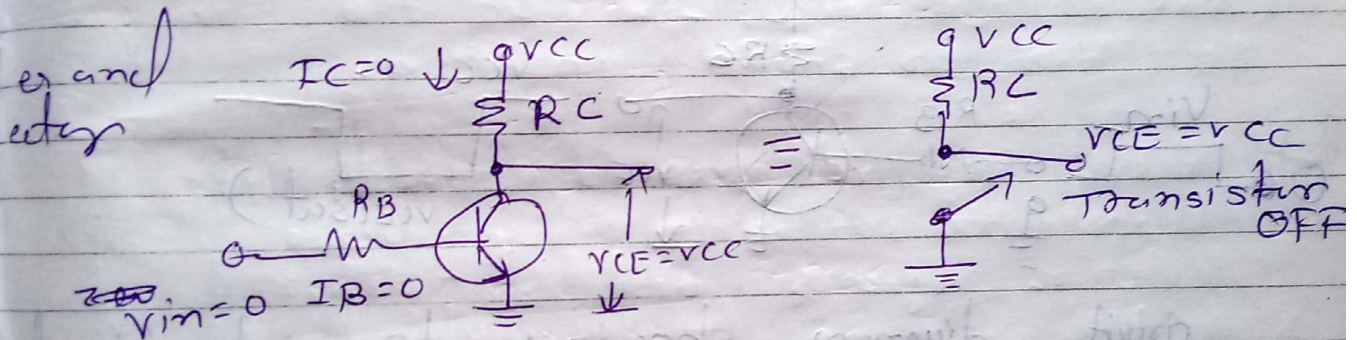1. Transistor in cutoff region
(Transistor as an open switch)

→ In cutoff region both the junctions of a transistor are reverse biased and a very small reverse current flows through the transistor


→ voltage drop across the transistor
 V_{CE} is high,
 $V_{in} = 0$, $I_B = 0$ and $I_C = 0$



(photo → Apply KVL to collector circuit of hundreds) fig
 $V_{CC} = I_C R_C + V_{CE}$
 $I_C = 0$
 $V_{CC} = V_{CE}$

for impedance so V_{CE} is high, $I_C = 0$. This matching shows that the resistance is infinite and transistor operates as open switch.

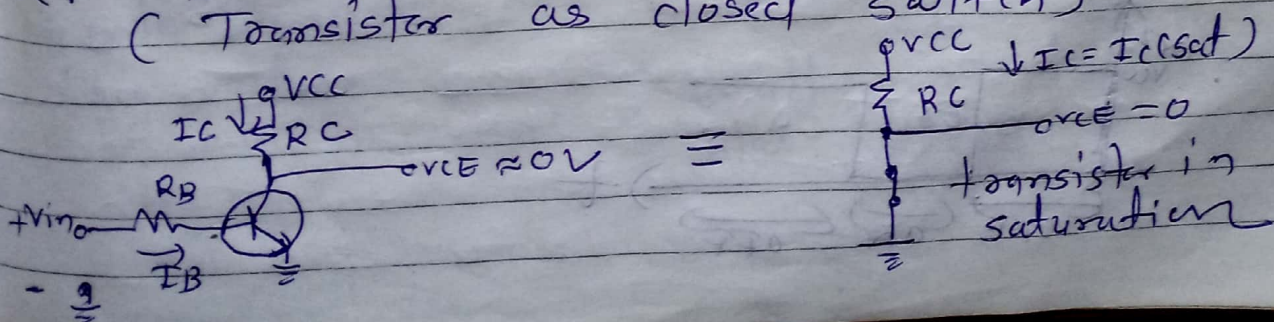2. Transistor in the saturation region
(Transistor as closed switch)




→ A high i/p voltage V_{in} is applied at the base.

→ The value of V_{in} and resistance R_B are adjusted such that a large I_B flows. This will saturate the transistor ($I_B > \frac{I_{C(sat)}}{\beta}$)

→ Both junctions are forward biased. The voltage drop V_{CE} is very small and I_C is very large.

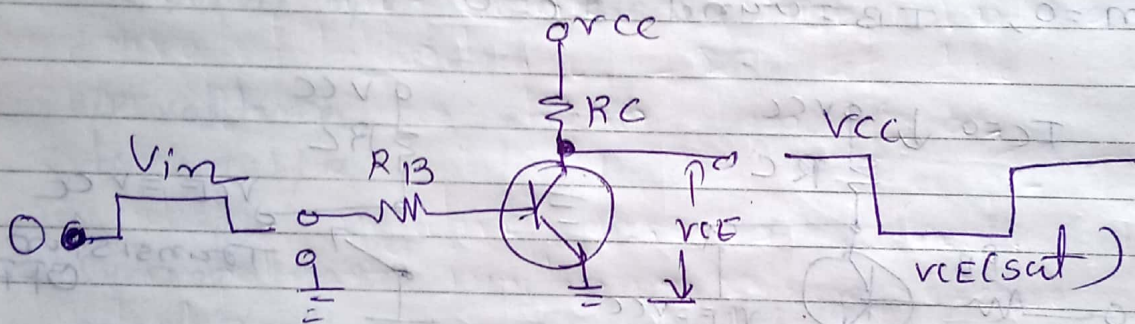
* Switching waveforms of an ideal transistor switch



circuit diagram showing transistor biased to operate as a switch.

→ when i/p is low (0), transistor is off, it acts as an open switch and $V_{CE} = V_{CC}$

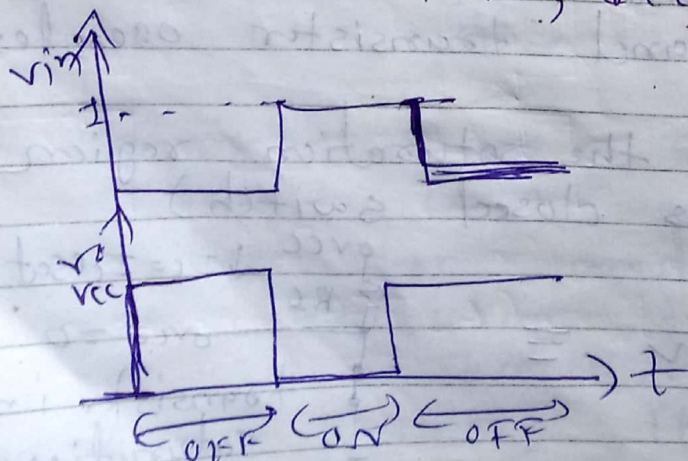→ i/p voltage goes high, transistor is driven into saturation, it acts as a closed switch, $V_{CE} = V_{CE(sat)} = 0V$.



Applications of

1. in the logic circuit
2. Temperature Controllers
3. Choppers used for DC motor control
4. Multivibrators and Schmitt trigger
5. Relay drivers
6. Stepper motor Controllers
7. Timers
8. SMPS and UPS.

Unit-5

field effect Transistors (FET) and its biasing

→ Junction field effect transistors

FET is a voltage operated device that can be used in amplifiers and switching circuits, same as BJT.

- Two categories of FET
junction FETs and MOSFETs

* N - (channel) JFET

